

Ohm's Law


Lab first

A resistor is a linear circuit element. The relationship between current and voltage for a resistor is a linear or directly proportional relationship. A graph of voltage and current gives a linear graph.

3 uses...

control current
to create heat
to create light

$$V = IR$$

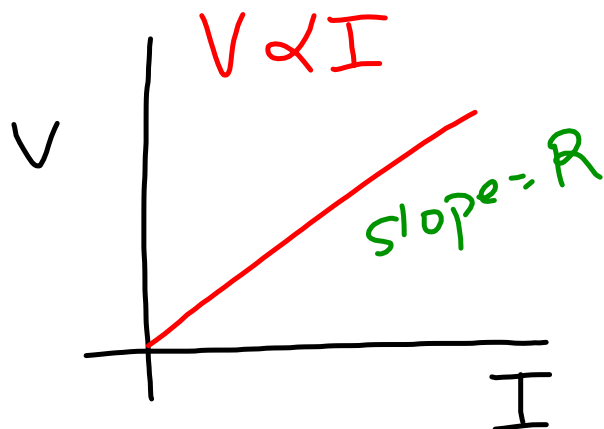

- 52.(c) A student measured the potential difference across, and the current through, two circuit elements, X and Y, and obtained the following data.

Element X		Element Y	
Potential difference (V)	Current (A)	Potential difference (V)	Current (A)
1	1	5	1
10	3	15	3
35	5	25	5

- (i) Draw a clearly labelled voltage vs. current graph for each element.
- (ii) Which element obeys Ohm's law? Explain.

- (iii) Calculate the resistance of the element in (ii).

Ohm's Law

$$V = IR$$

Current

$$I = \frac{Q}{t}$$

Voltage

$$V = \frac{EPE}{Q}$$

$$V = \frac{W}{Q}$$


Before we go any further, you need to practise...

Page 620 # 9, 10

Page 621 # 11, 13, 14, 23, 24, 25

Page 622 #35 a & b


Ohm's Law Worksheet

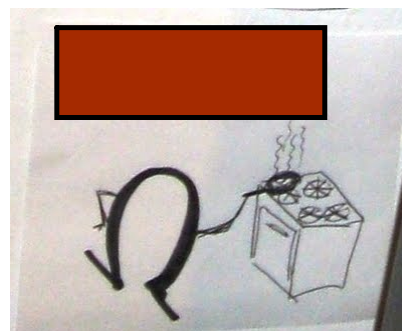

Summary to Date...we are making progress...!!!


	Series Circuits	Parallel Circuits
Voltage		
Current		

Kirchoff's Laws

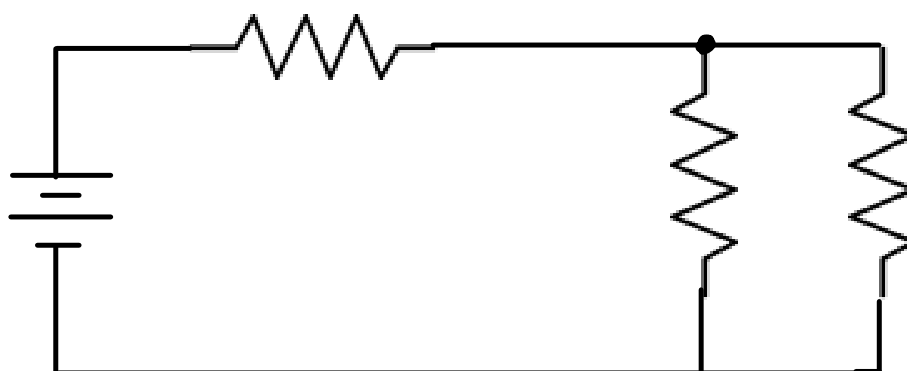


Kirchoff's Current Law

Kirchoff's Voltage Law

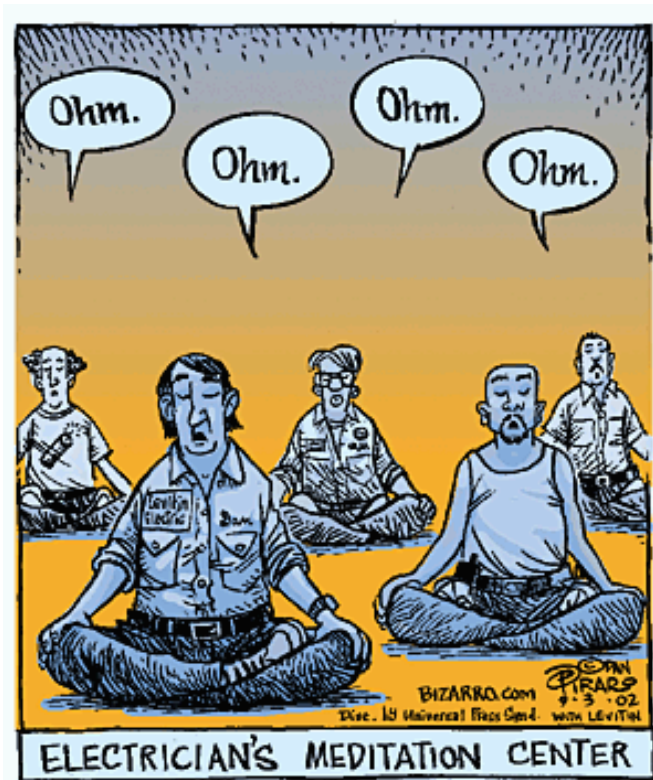


...Sample Circuits # 1-4

1.

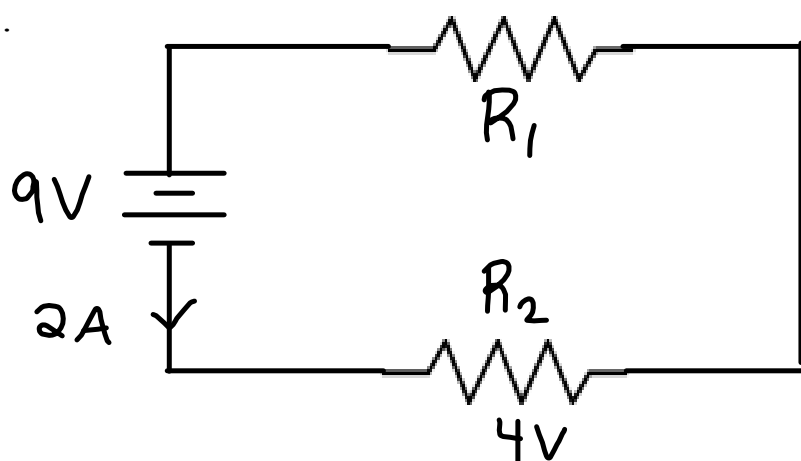



$V = IR$
I const. in series
V const. in parallel
KCL
KVL

2.

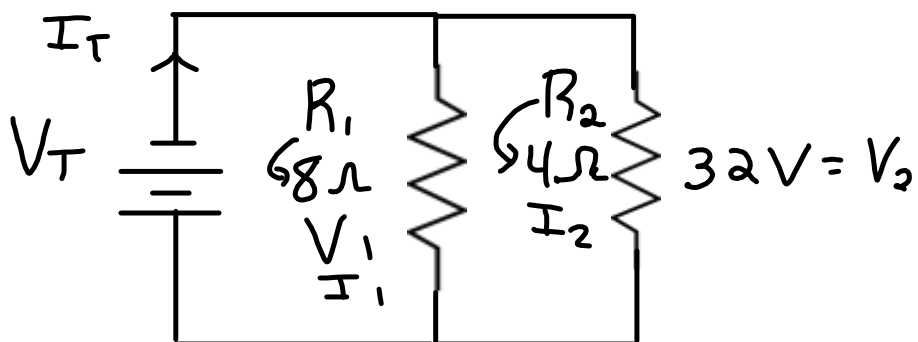


3.

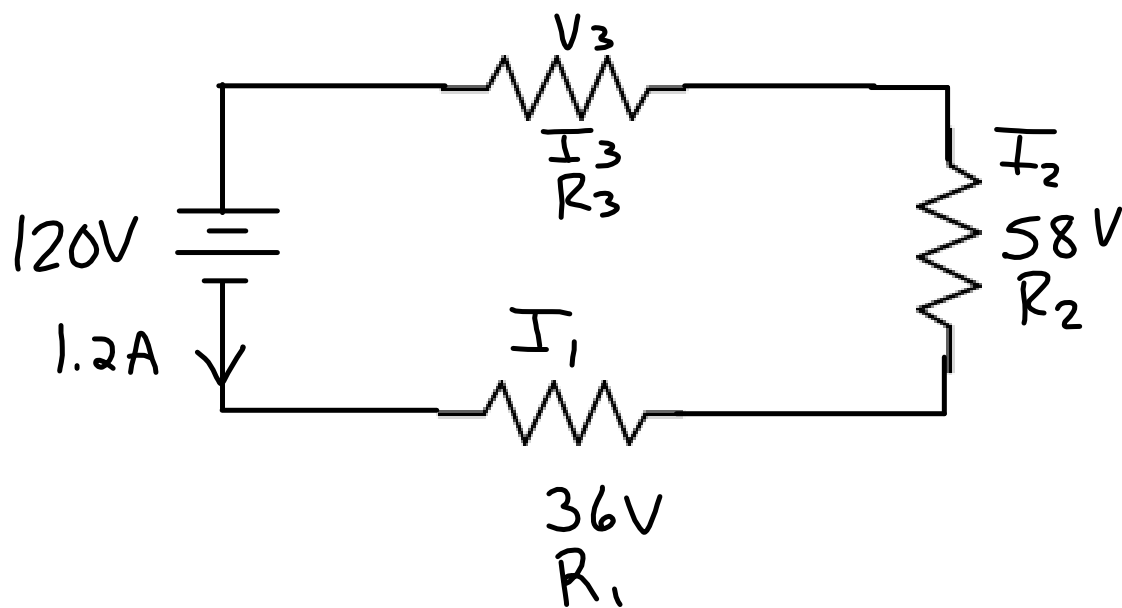

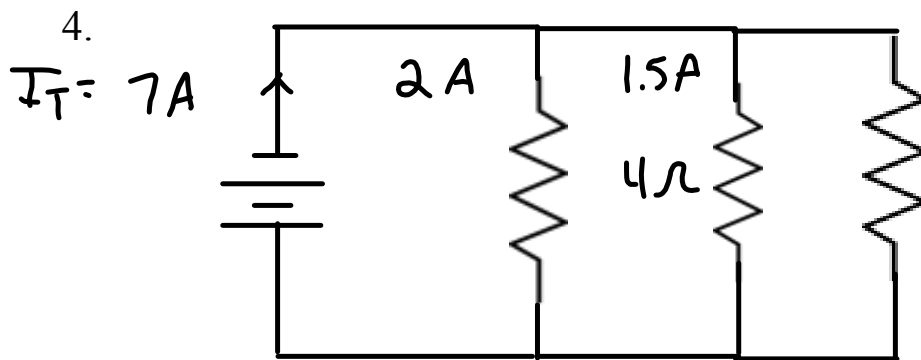

5.


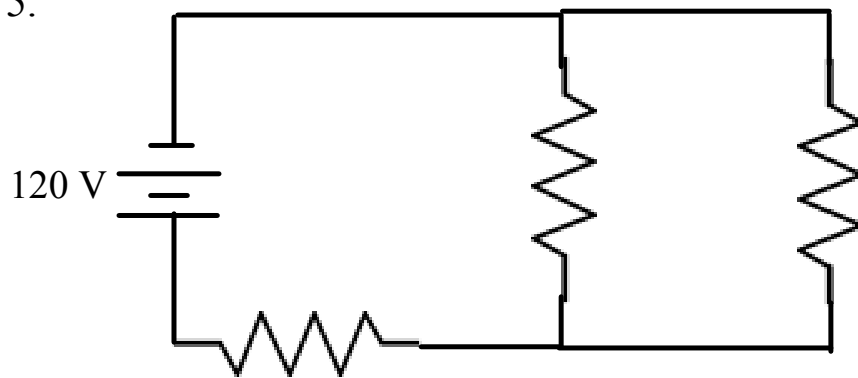



$$V_T = 5V$$

$$R_1 = 10\Omega$$

$$R_2 = 15\Omega$$

$$R_3 = 20\Omega$$

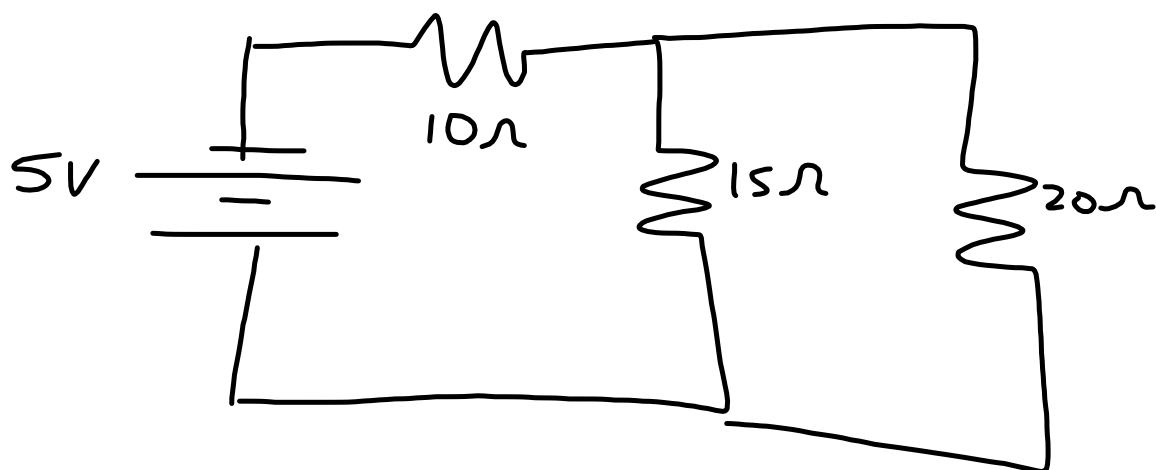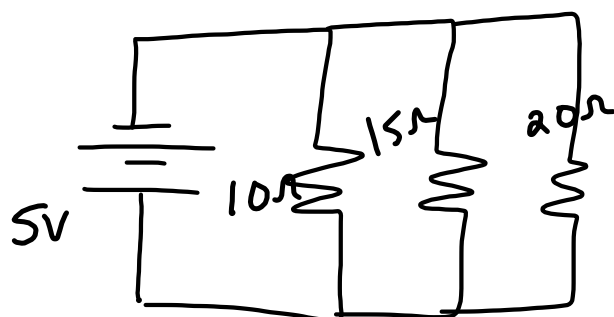

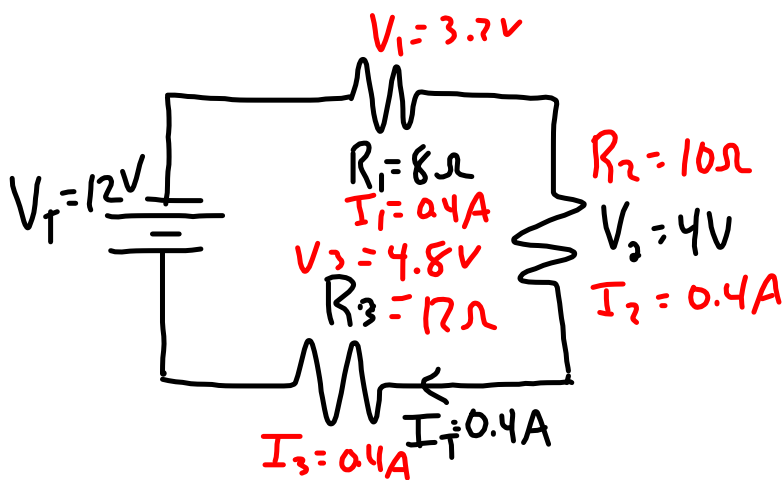

In series $\rightarrow I$ constant

In $\parallel \rightarrow V$ constant

$$V = IR$$

KVL

KCL

R_{eq}

$$I_1 = I_2 = I_3 = 0.4A \text{ (I const. in series)}$$

$$V_1 = I_1 R_1 \quad R_2 = \frac{V_2}{I_2}$$

$$V_1 = (0.4)(8) \quad R_2 = \frac{4}{0.4}$$

$$V_1 = 3.2V$$

$$R_2 = 10\Omega$$


$$V_{rises} = V_{drops} \text{ (KVL)}$$

$$12 = 3.2 + 4 + V_3$$

$$4.8V = V_3$$

$$R_3 = \frac{V_3}{I_3}$$
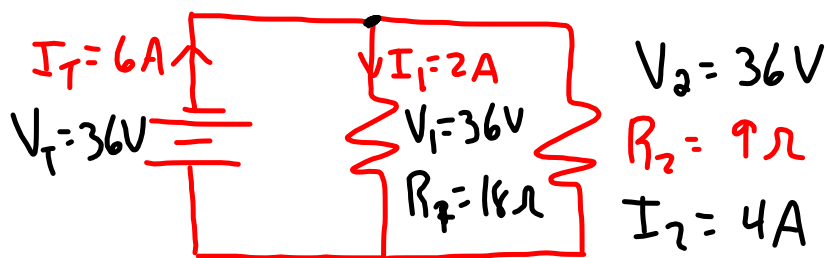
$$= \frac{4.8}{0.4} \rightarrow 12\Omega$$



$$(KCL) I_{in} = I_{out}$$

$$6 = 2 + I_2$$

$$4A = I_2$$


$$V_2 = I_2 R_2$$

$$V_2 = 4(9)$$

$$V_2 = 36V$$

$$V_1 = V_T = 36V \text{ (V const in parallel)}$$
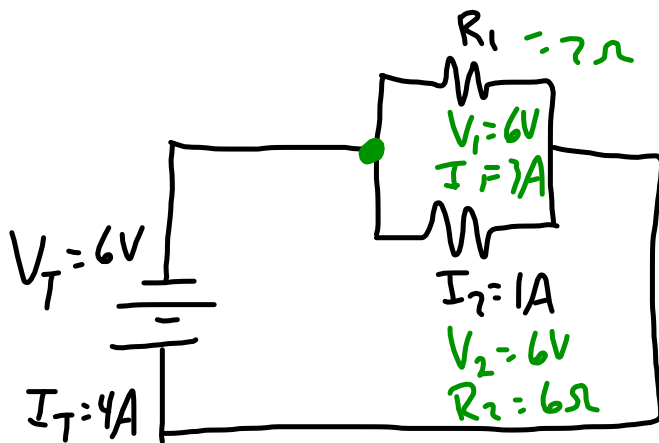
$$R_1 = \frac{V_1}{I_1} \Rightarrow \frac{36}{2} = 18 \Omega$$



$$V_1 = V_2 = 6V \text{ (V const. in parallel)}$$


$$R_2 = \frac{V_2}{I_2} \rightarrow \frac{6}{1} = 6\Omega$$

$$I_{in} = I_{out} \text{ (KCL)}$$

$$4 = I_1 + 1$$

$$I_1 = 3A$$
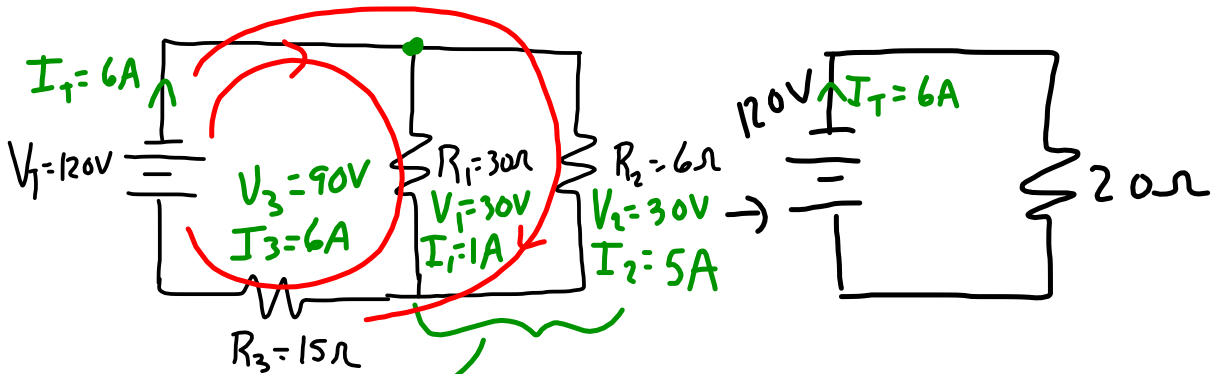
$$R_1 = \frac{V_1}{I_1} = \frac{6}{3} = 2\Omega$$



$$\frac{1}{R_{eq}} = \frac{1}{30} + \frac{1}{6}$$

$$\frac{1}{R_{eq}} = \frac{1+5}{30}$$

$$R_{eq} = 5\Omega$$

$$R_T = 15 + 5$$

$$R_T = 20\Omega$$

$$I_T = \frac{V_T}{R_T}$$

$$I_T = \frac{120}{20} = 6A$$

$$V_3 = I_3 R_3$$

$$V_3 = 6(15)$$

$$V_3 = 90V$$

$$(KVL) V_{rises} = V_{drops}$$

$$120 = V_1 + 90$$

$$V_1 = 30V$$

$$V_2 = 30V \text{ (V const. in parallel)}$$

$$I_1 = \frac{V_1}{R_1}$$

$$I_1 = \frac{30}{30}$$

$$I_1 = 1A$$

$$I_1 = \frac{V_1}{R_1} \text{ (KCL)}$$

$$I_{in} = I_{out}$$

$$6 = 1 + I_2$$

$$I_2 = 5A$$

$$I_3 = 6A \text{ (I const. in series)}$$

