

Power:

The rate at which energy is used or supplied.  
Power is measured in Watts (W).

$$P = \frac{\text{Energy}}{\text{time}}$$

Recall  $V = \frac{\text{Energy}}{\text{charge}}$                       so Energy = VQ


*Isn't math great...because now we get...*

$$P = \frac{VQ}{t} \quad \text{and} \quad P = VI$$

*Can you math types turn this into ...?*


$$P = I^2R \quad \text{and} \quad P = \frac{V^2}{R}$$

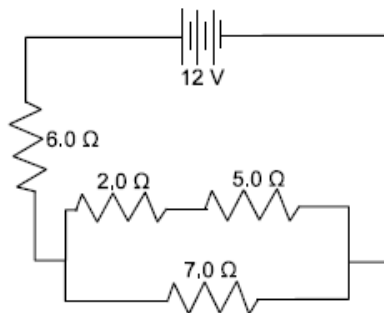52.(d) For the circuit shown in the diagram below, calculate:



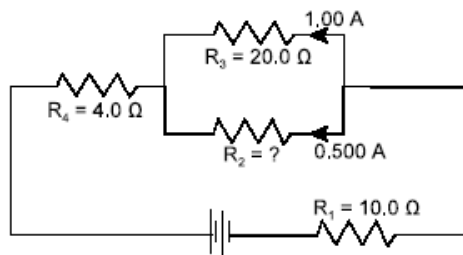- (i) the voltage across the 6.0 Ohm resistor;
- (ii) the current through the 5.0 Ohm resistor;
- (iii) the power dissipated in the 2.0 Ohm resistor.

6%52.(c) For the circuit below calculate:



- i) the value of  $R_2$ .
- ii) the power dissipated in  $R_4$ .
- iii) the voltage across the source.

iv) Explain how the addition of another resistor in parallel will change the total resistance of the circuit.

$V_T$  .  $V$

## Cost of Electrical Energy

We are charged for the energy we use and we use millions of Joules every day.

Since...

$$P = \frac{\text{Energy}}{\text{time}} \qquad \text{Energy} = P \times t$$

Since Joules are so small, Newfoundland Power charges for kilowatt-hours (kW-h). 1 kW-h = ? J

*get 2014 rates*

**Rate:** (Includes Municipal Tax and Rate Stabilization Adjustments)

Basic Customer Charge: .....\$15.68 per month

Energy Charge:

All kilowatt-hours .....@ 11.171 ¢ per kWh

Minimum Monthly Charge .....\$15.68 per month

How much would you be charged if you leave a 60W lightbulb on in your room while we are in Europe ( days)?

How much do you pay to use your 1500W hairdryer for 15 minutes each day for one month?

Determine the cost to operate a kettle on a 120V line for 1800h during the life of the kettle. The resistance of the element in the kettle is 9.6 Ohms.

At a cost of 9.339 cents/kWh how much will your radio add to your light bill if it draws 150mA on a 120V line and you leave it on during your 2 week vacation?



The dimmer switch on your overhead light has a resistance of 95 Ohms and 500mA passing through it. How much do you pay to use it for 3 1/2 hours per day for one month (30 days)?

Chi Straightener

1300w